

Universal gate Implementations

+ NAND implementation


① NOT gate




② AND gate



③ OR gate

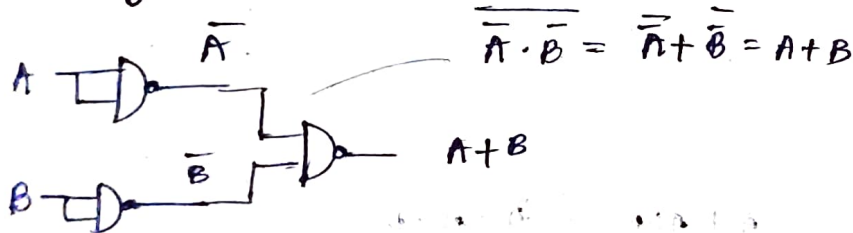

④ XOR gate

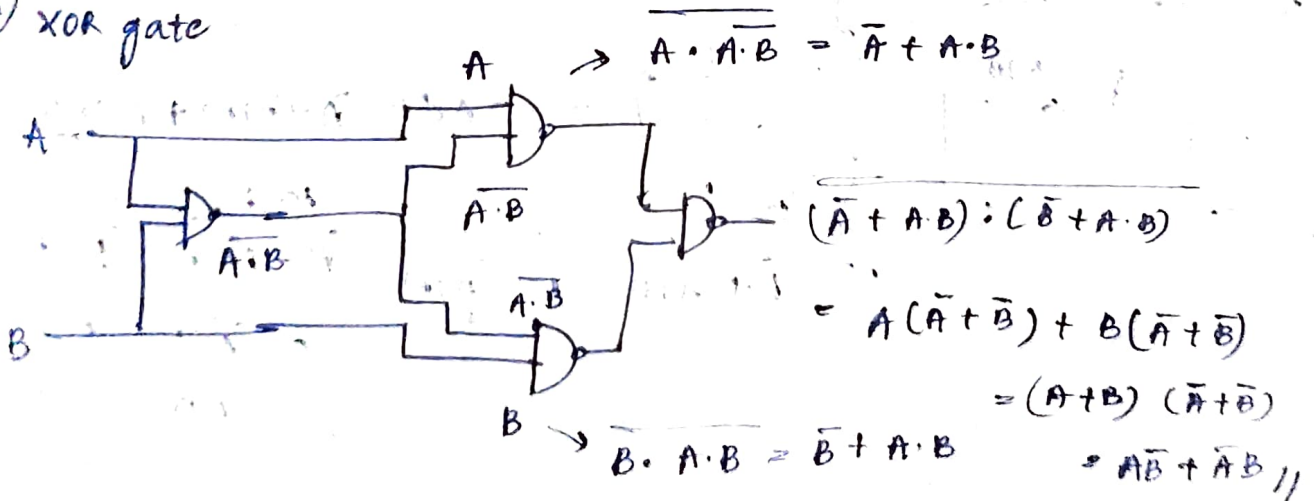

1940

100



1941-1942


$$\overline{A} \cdot (A + B)$$


1000

$$(A+B) \cdot (\bar{A} + \bar{B})$$

78.